

Student Names: Muhammet Ali Topcu

Section: 2

Group ID: 8

CMPE 240 Experiment 4 Preliminary Work

Truth Table:

#	CLK	X	Y	Z
0	0	0	0	x
1	1	0	0	0000
2	0	0	1	0000
3	1	0	1	0011
4	0	1	0	0011
5	1	1	0	0110
6	0	1	1	0110
7	1	1	1	1001

List of components used in the design:

1. 2 D Flip-flop
2. 3 AND Gate
3. 2 NOT Gate
4. 1 OR Gate
5. 1 Clock

Student Names: Muhammet Ali Topcu

Section: 2

Group ID: 8

Circuit:

